Mano 4-12 ~ 4-15

HDL Models of Comb Ckts
Behavioral Modeling
Writing a Simple Testbench
Logic Simulation

4-12 HDL Models of Combinational Ckts

* 1 module per file (.v) w/ the same name


Module:

- the basic building block for modeling hardware w/ the Verilog HDL
- Modeling styles of a module:
 - gate-level modeling: use instantiations of predefined and userdefined primitive gates
 - describes a ckt by specifying its gates and how they are connected w/ each other
 - dataflow modeling: use continuous assignment statements w/ the keyword assign
 - is used mostly for describing the Boolean equations of combinational logic
 - behavioral modeling: use procedural assignment statements w/
 the keyword always
 - is used to describe combinational and sequential ckts at a higher level of abstraction

Verilog Model for Combinational Logic

Figure 4.32

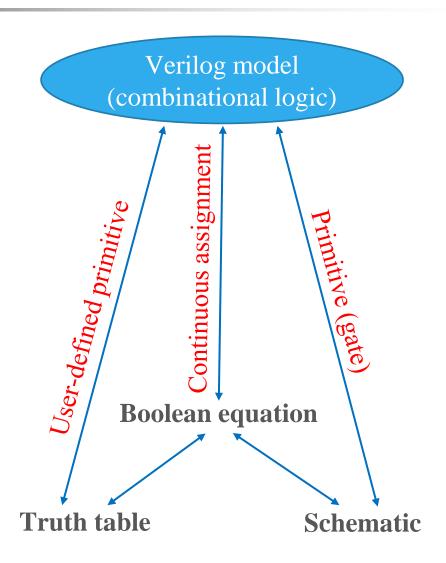Relationship of Verilog constructs to truth tables, Boolean equations, and schematics



A. Gate-Level Modeling

* The output of a primitive is always listed first in the port list, followed by the inputs.

- Gate-level modeling:
 - Provides a texture description of a *schematic diagram*.
 - A ckt is specified by its *logic gates* and *their interconnections*.
- Predefined primitives of gates in Verilog: 12
 - 8 digital logic primitive gates:

and, nand, or, nor, xor, nxor, not, buf

n-input 1-output primitives (can have any # of scalar inputs)

1-input *n*-output primitives (can drive multiple output lines)

- 4 three-state type primitive gates: p.HDL-47
 bufif1, bufif0, notif1, notif0
- * The logic of each gate is based on a 4-valued system: 0, 1, x (unknown), z (high impedance)

4-Valued System

- **0**
- **1**
- **x**: unknown
 - An unknown value is assigned during simulation when the logic value of a signal is ambiguous (can not be determined whether its value is 0 or 1).
- **z**: high impedance
 - occurs at the *output of three-state gates that are not* enabled or if a wire is inadvertently left unconnected.
- E.g.: 4-valued logic truth tables (p.208, Table 4.9)

4-Valued Logic Truth Tables

■ E.g.: 4-valued logic truth tables (p.208, Table 4.9)

Truth Table for Predefined Primitive Gates

and	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X


or	0	1	X	Z
0	0	1	X	X
1	1	1	1	1
X	X	1	X	X
Z	X	1	X	X

xor	0	1	X	Z
0	0	1	X	X
1	1	0	X	X
X	X	X	X	X
Z	X	X	X	X

not	input	output
	0	1
	1	0
	X	X
	Z	X

HDL Example 4.1: 2-to-4 Line Decoder

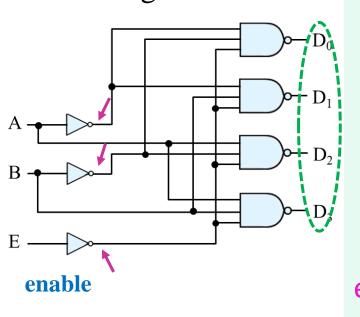- HDL Example4.1: 2-to-4 LineDecoder
 - gate-leveldescription ofFig 4.19



```
module decoder 2x4 gates (D, A, B, enable);
  output [0:3] D;
  input
                A, B;
  input
                 enable;
  wire
                 A_not, B_not, enable_not;
  not
                           The keyword not may
   G1 (A_not, A),
                           be written only once for
                           the three gates.
   G2 (B_not, B),
   G3 (enable_not, enable);
  nand
   G4 (D[0], A_not, B_not, enable_not),
   G5 (D[1], A_not, B, enable_not),
   G6 (D[2], A, B_not, enable_not),
   G7 (D[3], A, B, enable_not);
endmodule
```

4

• vector:

- a multiple-bit width identifier
- e.g.s:

```
output [0: 3] D;wire [7: 0] SUM;
```

```
module decoder 2x4 gates (D, A, B, enable);
 output [0:3] D;
 input
                A, B;
                enable;
 input
 wire
                A not, B not, enable not;
 not
   G1 (A not, A),
   G2 (B_not, B),
   G3 (enable not, enable);
 nand
   G4 (D[0], A not, B not, enable not),
   G5 (D[1], A not, B, enable not),
   G6 (D[2], A, B_not, enable_not),
   G7 (D[3], A, B, enable not);
endmodule
```

- includes within "[]" 2 numbers separated w/ a ":"
 - The 1st number listed is always the MSB of the vector.
 - The individual bits are specified within [], D[2].
 - > may address parts (contiguous bits) of vectors, SUM[2: 0].
- wire: for internal connections
- * The output is always listed first in the port list of a primitive, followed by the inputs.

Design Methodologies of Digital Circuits

- 2 basic design methodologies: hierarchical
 - bottom-up design: the building blocks are first identified and then combined to build the top-level block
 - > E.g.:

```
Half adder (HA): add two bits, 1 XOR gate + 1 AND gate
```

- \Rightarrow Full adder (FA): add three bits, 2 HAs + 1 OR gate
- \Rightarrow *n*-bit ripple-carry adder (RCA): add 2 *n*-bit numbers, *n* FAs
- top-down design: the top-level block is defined and then the subblocks necessary to build the top-level block are identified
 - > E.g.:

```
n-bit ripple-carry adder (RCA) \Rightarrow n full adders (FAs)
Full adder \Rightarrow 2 half adders (HAs) + 1 OR gate
```

Half adder \Rightarrow 1 XOR gate + 1 AND gate

J.J. Shann HDL-9


HDL Example 4.2: Ripple-Carry Adder

■ HDL Example 4.2: 4-bit Ripple-Carry Adder

- gate-level description
- bottom-uphierarchicaldescription:


$$HA \rightarrow FA \rightarrow RCA$$

– HA: Fig 4.5(b)

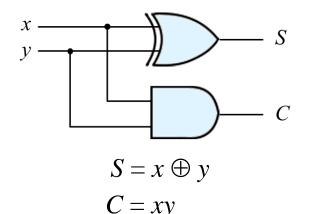
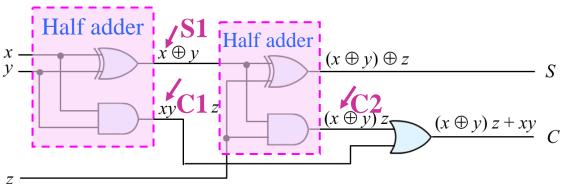
```
// Description of half adder
// module half_adder (S, C, x, y);
// output
           S, C;
// input x, y;
// Alternative Verilog 2005 syntax:
module half_adder (output S, C, input x, y);
// Instantiate primitive gates
  xor (S, x, y);
  and (C, x, y);
endmodule
```






HA module

```
module half_adder (output S, C, input x, y);
xor (S, x, y);
and (C, x, y);
endmodule
```

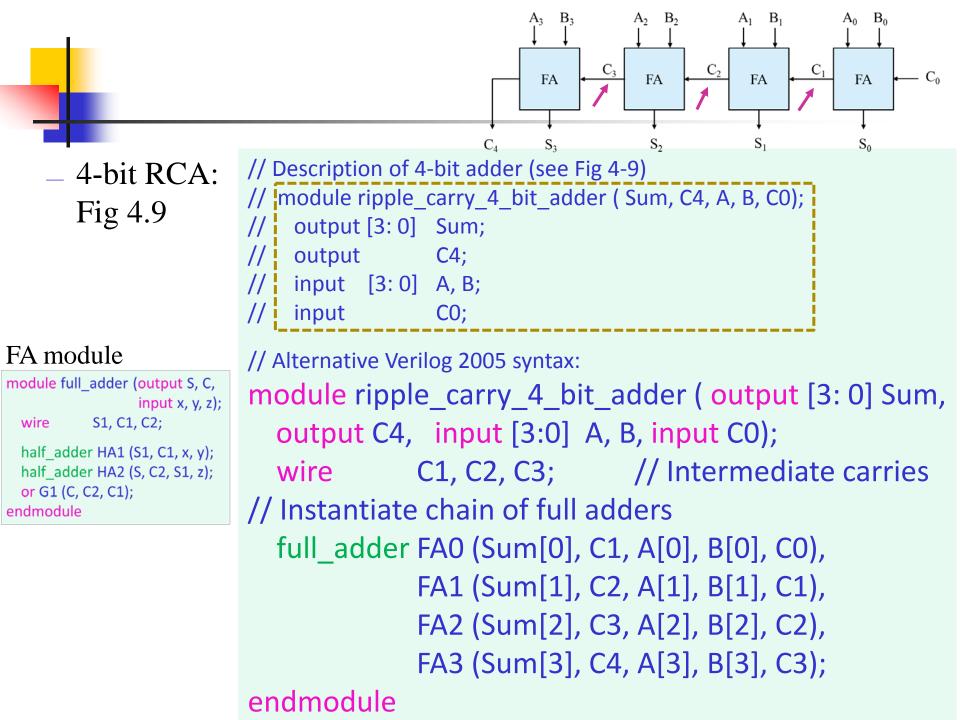
```
// Description of full adder
// module full_adder (S, C, x, y, z);
// output S, C;
// input x, y, z;
// alternative Verilog 2005 syntax:
module full adder (output S, C, input x, y, z);
             S1, C1, C2;
  wire
// Instantiate half adders
  half_adder HA1 (S1, C1, x, y);
  half_adder HA2 (S, C2, S1, z);
  or G1 (C, C2, C1);
endmodule
```



- 4
 - Module declarations cannot be nested.
 - A module definition (declaration) cannot be placed within another module declaration.
 - ⇒ A module definition cannot be inserted into the text b/t the module and endmodule keywords of another module.
 - Modules can be instantiated within other modules.
 - Creates a *hierarchical* decomposition of a design.
 - \Rightarrow *structural* description
 - * One module per file (.v) & w/ the same name.

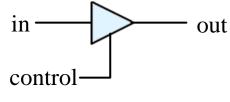B. Three-State Gates


- Three-state gate:
 - has a control input that can place the gate into a *highimpedance* state (z).
- Types of three-state gates: 4
 - bufif1
 - bufif0




in out


– notif0

notif1

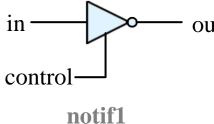

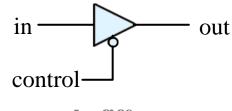




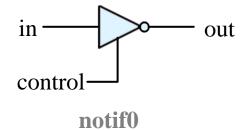



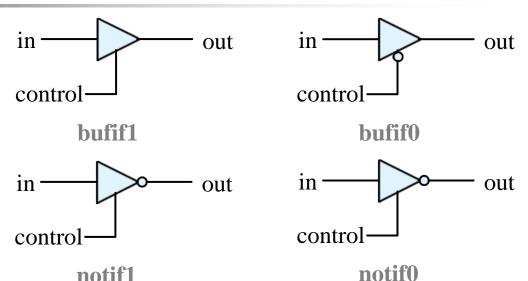- Three-state gates:
 - bufif1, bufif0,notif1, notif0




- are instantiated w/ the statement
 - gate name (output, input, control);
- In simulation, the output can result in 0, 1, x, or z.
- The outputs of 3-state gates can be connected together to form a common output line.

HDL Example: 2-to-1 Line Multiplexer

- HDL Example: 2-to-1
 Line MUX w/ three-state
 buffers
 - p.205, Fig 4.30
 - tri: for tristate
 - indicate that the output has multiple drivers
 - Types of 3-state gates:bufif1, bufif0, notif1, notif0
 - Instantiate of a 3-state gate:

gate name (output, input, control);

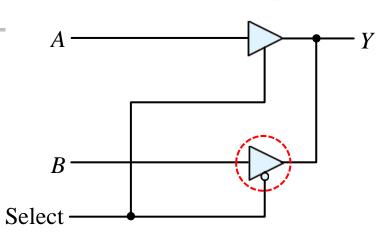

```
module mux_tri (m_out, A, B, select);
  output m_out;
  input A, B, select;
  tri m_out;

bufif1 (m_out, A, select);
  bufif0 (m_out, B, select);
endmodule
```



- nets: a class of data types
 - represent connections b/t hardware elements



 If an identifier is used, but not declared, the language specifies that it will be interpreted (by default) as a wire.

C. Dataflow Modeling

	Bitwise	Logical
AND	&	&&
OR		
NOT	~	!

Dataflow modeling:

- uses a number of operators that act on binary operands to produce a binary result.
- Commonly used Verilog HDL operators: p.222, Table 4.10

Commonly used Verilog HDL operators: Table 4.10

Symbol	Operation	Symbol	Operation
+	binary addition		
_	binary subtraction		
&	bitwise AND	&&	logical AND
	bitwise OR		logical OR
^	bitwise XOR		
~	bitwise NOT	!	logical NOT
==	equality		
>	greater than		
<	less than		
{}	concatenation		
?:	conditional		V.V. 171191111

DL-19

	Symbol	Operation	Symbol	Operation
	+	binary addition		
	_	binary subtraction		
	&	bitwise AND	&&	logical AND
i		bitwise OR		logical OR
1	٨	bitwise XOR		
	~	bitwise NOT	!	logical NOT
	==	equality		
	>	greater than		
	<	less than		
	{}	concatenation		
	?:	conditional		

	Bitwise	Logical
AND	&	&&
OR		
NOT	~	!

- bitwise operators: operate bit by bit on a pair of vector operands to produce a vector result
 - E.g.: ~(1010) is (0101)
- logical operators:
 - E.g.: !(1010) is 0

- * If the operands are *scalar*, the results of *bitwise* and *logical* operators will be identical; if the operands are **vectors**, the result will not necessarily match.
- concatenation operator: {}, append multiple operands
- conditional operator: ?:, acts like a multiplexer

condition? true-expression: false-expression

*	If the operands are scalar, the results will
	be identical; if the operands are vectors,
	the result will not necessarily match.

	Bitwise	Logical
AND	&	&&
OR		
NOT	~	!


- Example: A = 1010, B = 0000
 - -A has the Boolean value 1, B has Boolean value 0.
 - Results of other operations with these values:

A & B = 0000	// Bitwise AND	(1010) & (0000) = (0000)
A && B = 0	// Logical AND	(1010) && (0000) = 0
$A \mid B = 1010$	// Bitwise OR	$(1010) \mid (0000) = (1010)$
$A \parallel B = 1$	// Logical OR	$(1010) \parallel (0000) = 1$
$\sim A = 0101$	// Bitwise negation	\sim (1010) = (0101)
!A = 0	// Logical negation	!(1010) = !(1) = 0
\sim B = 1111	// Bitwise negation	\sim (0000) = (1111)
!B = 1	// Logical negation	!(0000) = !(0) = 1
(A > B) = 1	// is greater than	
(A == B) = 0	// identity (equality)	J.J. Shann HDL-24

Dataflow Modeling of Comb. Logic

- Dataflow modeling of combinational logic:
 - Describes combinational ckts by their *function* rather than by their gate structure
 - uses *continuous assignments* and the keyword **assign**.
 - E.g.: a 2-to-1-line MUX w/ scalar data inputs A and B,


select input S, and output Y

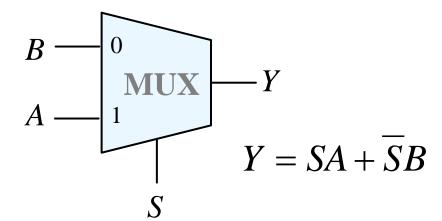

	Bitwise	Logical
AND	&	&&
OR		
NOT	~	!

HDL Example 4.3: 2-to-4 Line Decoder (Dataflow)

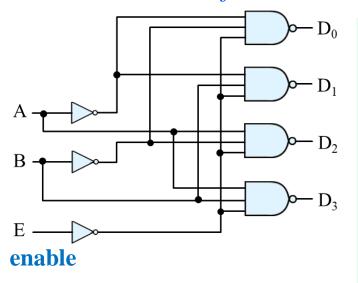- HDL Example 4.3: (Dataflow)
 - dataflow description of Fig 4.19




	Bitwise	Logical
AND	&	&&
OR		
NOT	~	!

```
//Verilog 2001, 2005 Syntax
module decoder_2x4_df (
  output [0: 3] D,
  input
              A, B,
                 enable
  input
  assign D[0] = !((!A) \&\& (!B) \&\& (!enable)),
           D[1] = !((!A) \&\& B \& (!enable)),
           D[2] = !(A \&\& (!B) \&\& (!enable)),
           D[3] = !(A \& B \& \& (!enable));
endmodule
```

HDL Example 4.4: 4-bit Adder (Dataflow)

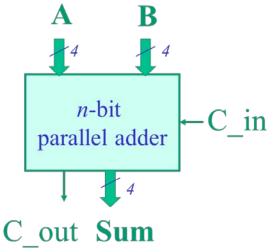- HDL Example 4.4: (Dataflow) 4-bit adder
 - dataflow description of 4-bit adder




		_	
Symbol	Operation	Symbol	Operation
+	binary addition		
_	binary subtraction		
&	bitwise AND	&&	logical AND
	bitwise OR	İ II	logical OR
À	bitwise XOR	j "	
~	bitwise NOT	!!	logical NOT
==	equality	İ	
>	greater than	ĺ	
<	less than	ĺ	
{}	concatenation	ĺ	
?:	conditional	İ	

```
// Verilog 2005 module port syntax
module binary_adder (
   output [3:0] Sum,
                 C out,
   output
   input [3: 0] A, B,
   input
                  C in
 assign({C_out, Sum} = A + B + C_in;
endmodule
   5-bit result of the addition operation
                          J.J. Shann HDL-27
```

HDL Example 4.5: 4-bit Comparator (Dataflow)

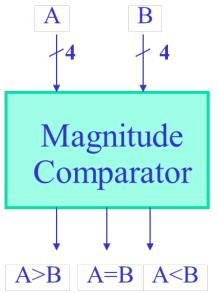■ HDL Example 4.5: (Dataflow) 4-bit comparator




Symbol	Operation	Symbol	Operation
+	binary addition		
_	binary subtraction		
&	bitwise AND	&&	logical AND
	bitwise OR		logical OR
٨	bitwise XOR		_
~	bitwise NOT	!!	logical NOT
==	equality		
>	greater than		
<	less than		
{}	concatenation		
?:	conditional		

```
// Verilog 2001, 2005 syntax
module mag_compare (
  output A_lt_B, A_eq_B, A_gt_B,
  input [3: 0] A, B
  assign A_{t_B} = (A < B);
  assign A_gt_B = (A > B);
  assign A eq B = (A == B);
endmodule
```

HDL Example 4.6: 2-to-1 MUX (Dataflow)

■ HDL Example 4.6: (Dataflow) 2-to-1 MUX

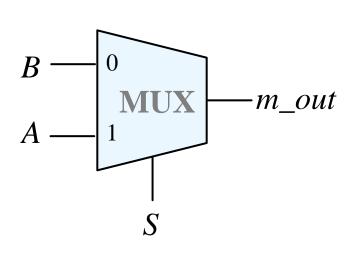

```
// Verilog 2001, 2005 syntax
module mux_2x1_df(m_out, A, B, select);
output m_out;
input A, B;
input select;

assign m_out = (select)? A : B;
endmodule
```

— conditional operator: ?:
condition ? true-expression : false-expression

D. Behavioral Modeling

* reg data type:
retains its value until a
new value is assigned

Behavioral modeling:

- represents digital ckts at a functional and algorithmic level
- is used mostly to describe sequential ckts, but can also be used to describe combinational ckts.
- use keyword always, followed by an optional event control expression and a list of procedural assignment statements.

```
always @ (event control expression) begin
//procedural assignment statements
end specifies when the statements will execute
```

- The procedural assignment statements inside the always block are executed every time there is a change in <u>any</u> of the variables listed after the @ symbol. <u>keyword or</u>
- * The target output of the procedural assignment statement must be **reg** data type.

 J.J. Shann HDL-30

- 4
 - if-else conditional statement
 - case statement: case ... endcase
 - a multiway conditional branch construct
 - The case items have an implied priority because the list is evaluated from top to bottom.

HDL Example 4.7: 2-to-1 MUX (Behavioral)

- HDL Example 4.7: (Behavioral) 2-to-1 Line MUX
 - Behavioral description of 2-to-1 line MUX

```
B \longrightarrow 0
A \longrightarrow 1
S \longrightarrow m_out
```

```
// Verilog 2001, 2005 syntax
                              * The target output
module mux 2x1 beh(
                                of the procedural
  output (reg)m_out,
                                assignment
                                statement inside
               A, B, select
  input
                                always must be reg
                                data type.
  always @(A or B or select)
                                //@(A, B, select)
    if (select == 1) m_out(=)A;
                                //(select)
    else m_out(=)B;
```

if-else conditional statement

endmodule

* Use blocking assignments (=) in always block for combinational logic.

HDL Example 4.8: 4-to-1 Line MUX (Behavioral)

- HDL Example 4.7: (Behavioral) 4-to-1 Line MUX
 - Behavioraldescription of 4-to-1line MUX

```
// Verilog 2001, 2005 syntax
module mux_4x1_beh
(output reg m out,
             in_0, in_1, in_2, in_3,
 input
 input [1:0] select
);
 always @(in_0, in_1, in_2, in_3, select)
    case (select)
     \sqrt{2'}b00; m_out = in_0;
      2'b01: \m_out = in_1;
     2'b10: / m_out = in_2;
     2'b11! \le m_out = in 3;
    endcase
                case items, have implied
endmodule
                  priority (top to bottom)
```


case Construct

- case statement: case ... endcase
 - a multiway conditional branch construct
 - The case items have an implied priority because the list is evaluated from top to bottom.
- default: the last item in the list of case items, for unlisted case items
- 2 important variations of case construct:
 - casex: don't-cares any bits of the case expression or the
 case item that have logic value x or z
 - casez: don't-cares only the logic value z

x: unknown


z: high-impendence

Numbers

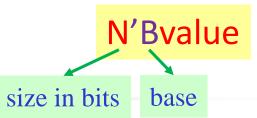

- Numbers can be specified in *binary*, *octal*, *decimal*, or *hexadecimal* (bases 2, 8, 10, 16):
 - Underscores (_) in numbers are ignored and can be helpful in breaking long numbers into more readable chunks.
- Format for declaring constants: N'Bvalue
 - N: the size in bits, leading zeros are inserted to reach this size
 - optional, but better give the size explicitly.
 - If the size is not specified, the system assumes that it is the word length of the host simulator or at least 32 bits.
 - B: the letter indicating the base
 - > 'b for binary, 'o for octal, 'd for decimal, and 'h for hexadecimal
 - If the base is omitted, it defaults to decimal.
 - value: gives the value



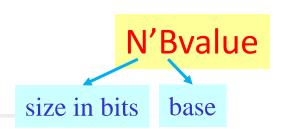

Examples: Harris, Table 4.3, p.180

Numbers	Bits	Base	Val	Stored
3'b101	3	2	5	101
'b11	?	2	3	000011
8'b11	8	2	3	00000011
8'b1010_1011	8	2	171	10101011
3'd6	3	10	6	110
6'042	6	8	34	100010
8'hAB	8	16	171	10101011
42	?	10	42	0000101010

Summary

- Guidelines of modeling combinational logic:
 - Gate-level modeling
 - Dataflow modeling:
 - Use continuous assignments assign to model simple combinational logic.
 - Behavioral modeling:
 - Use always @ (*) and blocking assignments to model more complicated combinational logic where the always statement is helpful.
 - * Do not make assignments to the same signal in more than one always statement or continuous assignment statement.

```
assign y = s ? d1 : d2;
```


```
always @ (*)
begin


p = a ^ b; //blocking
q = a & b; //blocking
s = p ^ cin;
cout = q | (p & cin);
end
```

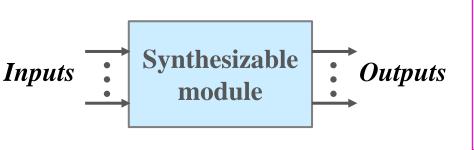E. Writing a Simple Test Bench

Test bench:

- is an HDL program used for describing and applying a stimulus to an HDL model of a ckt in order to test it and observe its response during simulation.
- Write stimuli that will test a ckt thoroughly, exercising all
 of the operating features that are specified.
- can be complex and lengthy and may take longer to develop than the design that is tested.
- The results of a test are only as good as the test bench that is used to test a ckt.



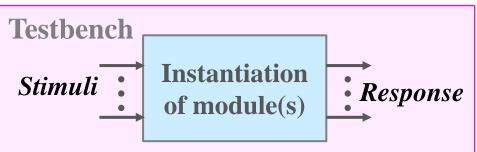

(a) Providing Input Stimulus

- Statements used by a test bench to provide a stimulus to the ckt being tested:
 - initial statement: executes only once
 - starting from simulation time 0, and may continue w/ any operations that are delayed by a given number of time units, as specified by the symbol #.
 - always statement: executes repeatedly in a loop
 - specify how the associated statement is to execute (the *event control expression*)

```
always @ (event control expression) begin
//procedural assignment statements
end
```



Example:

stimulus A B

$$(t = 0)$$
 0 0

$$(t = 10)$$
 1 0

$$(t = 30)$$
 0 1

Example:

stimulus D

$$(t = 0)$$
 000

$$(t = 10)$$
 001

. . .

$$(t = 70)$$
 111

Initial begin

```
A = 0; B = 0;
#10 A = 1;
#20 A = 0; B = 1;
end
```


Initial begin D = 3'b000;

```
repeat (7)
#10 D = D + 3'b001;
end
```

repeat: specifies a looping statement

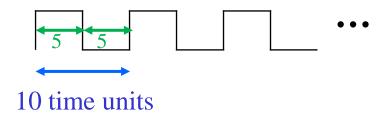Example:

generate periodic clock pulse (period = 10 time units)



```
always
  begin
  clock = 1; #5; clock = 0; #5;
  end
```

(b) Displaying Output Response to the Stimulus

- The response of the stimulus generated by the initial and always blocks will appear:
 - in text format as standard output &
 - as waveforms (timing diagrams) in simulators having graphical output capability
- Numerical outputs are displayed by using Verilog system tasks.
- Verilog system tasks:
 - are built-in system functions that are recognized by keywords that begin with the symbol \$.

System Tasks for Display

- \$\int \text{\$display}\$: display a one-time value of variables or strings with an end-of-line return
- **\$write**: same as **\$display**, but w/o going to next line
- \$monitor: display variables whenever a value changes during a simulation run
- **\$time**: display the *simulation time*
- **\$finish**: terminate the simulation

Syntax for \$display, \$write, and \$monitor: (next page)

Syntax for \$display, \$write, and \$monitor:

Task-name (format specification, argumentlist);

- format specification:
 - uses the symbol % to specify the radix of the numbers that are displayed: %b, %d, %h, %o (%B, %D, %H, %O)
 - may have a string enclosed in quotes (".....")
 - > No commas in the format specification.

– argument list:

- has commas b/t the variables.
- _ E.g.s:


```
$display ("%d %b %b", C, A, B);
```


\$display ("time = %0d A = %b B = %b", \$time, A, B);

format specification

%d: w/ the leading spaces%0d: w/o the leading spaces

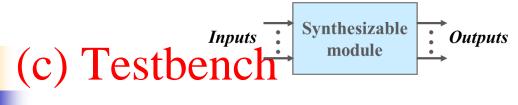* In displaying time values, use the format %0d instead of %d. (Time is calculated as a 32-bit number.)



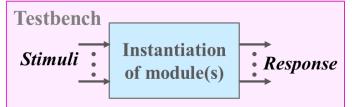


Form of a test bench:

```
module test_module_name; //no port list
   //Declare local reg and wire identifiers.
   //Instantiate the design module(s) under test.
   //Specify a stopwatch, using $finish to terminate the simulation.
   //Generate stimulus, using initial and always statements.
   //Display the output response (text or graphics, or both).
endmodule
```

- has no inputs or outputs \Rightarrow No port list!
- The signals that are applied as inputs to the design module for simulation are declared in the stimulus module as local reg data type.
- The outputs of the design module that are displayed for testing are declared in the stimulus module as local wire data type.

J.J. Shann HDL-45

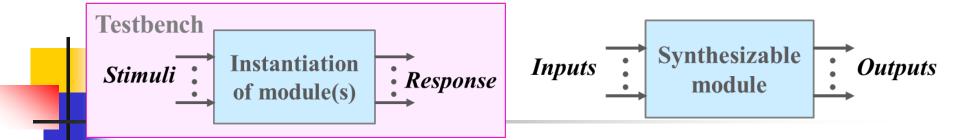

Interaction b/t stimulus and design modules:

Stimulus module (testbench)

```
module t_circuit;
 reg t_A, t_B;
  wire t_C;
  parameter stop_time = 1000;
 circuit M (t_C,(t_A, t_B);
// Stimulus generators for t_A and t_B
 initial # stop_time $finish;
endmodule
```


Design module

```
module circuit (C, A, B);
input A, B;
output C;

// Description of the module
endmodule
```

HDL Example 4.9: Test Bench (2-to-1 MUX)

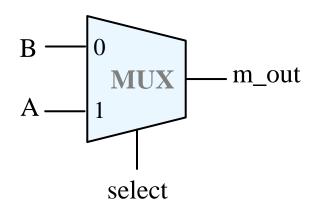HDL Example 4.9: Test bench w/ stimulus for mux_2x1_df



```
module mux_2x1_df(m_out, A, B, select);
  output m_out;
  input A, B;
  input select;
  assign m_out = (select)? A : B;
  endmodule
```

```
module t_mux_2x1_df;
  wire t_m_out;
                           parameter: a keyword,
          t_A, t_B;
                           defines constant
  reg
          t_select;
  reg
  parameter stop_time = 50;
  // Instantiation of circuit to be tested
  mux_2x1_df M1 (t_m_out, t_A, t_B, t_select);
  initial # stop_time $finish;
                           $finish: a system task,
  // Stimulus generator
                           terminates the simulation
  initial begin
    t_select = 1; t_A = 0; t_B = 1;
         t A = 1; t B = 0;
                             Stimulus: Select A
    #10 t select = 0;
                             (t = 0)
                             (t = 10) 1 1 (t = 20) 0 1
    #10 t_A = 0; t_B = 1;
  end
                              (t = 30)
```

```
module mux_2x1_df(m_out, A, B, select);
output m_out;
input A, B;
input select;
assign m_out = (select)? A : B;
endmodule

module t_mux_2x1_df(m_out, A, B, select);
Select
Select
Select
Select
Selec
```

Simulation log: Select = 1 A = 0 B = 1 OUT = 0 time = 0Select = 1 A = 1 B = 0 OUT = 1 time = 10Select = 0 A = 1 B = 0 OUT = 0 time = 20Select = 0 A = 0 B = 1 OUT = 1 time = 30

```
//Declaration of local identifiers
  // Instantiation of circuit to be tested
  // Stimulus generator
                                                    $monitor: a system task,
                           $display: a system task,
                                                    displays the output
                            print in the simulator
  //Response monitor
                                                    caused by the given
                            window
  initial begin
                                                    stimulus
    $display (" time Select A B m_out");
    $monitor ($time, " %b %b %b %b", t_select, t_A, t_B, t_m_out);
    //$monitor ("time=", $time, "select = %b A = %b B = %b m out = %b",
    t_select, t_A, t_B, t_m_out);
  end
endmodule
```

HDL Example 4.10: Design Module & Test Bench (1/2)

- HDL Example 4.10:
 Design Module &
 Test bench of Fig 4.2
 - gate-level descriptionof ckt of Fig 4.2

```
module Circuit_of_Fig_4_2 (
  output F1, F2,
  input A, B, C);
 wire T1, T2, T3, F2_not, E1, E2, E3;
  or G1 (T1, A, B, C);
  and G2 (T2, A, B, C);
  and G3 (E1, A, B);
  and G4 (E2, A, C);
 and G5 (E3, B, C);
  or G6 (F2, E1, E2, E3);
  not G7 (F2 not, F2);
  and G8 (T3, T1, F2_not);
  or G9 (F1, T2, T3);
endmodule
```

HDL Example 4.10: Design Modul Bench (2/2)

reg [2: 0] D;

module t_Circuit_of_Fig_4_2;

D[1], D[0], F1, F2);

end

endmodule

Stimulus to analyzethe ckt of Fig 4.2

```
module Circuit of Fig 4 2 (
  output F1, F2,
 input A, B, C);
  wire T1, T2, T3, F2 not, E1, E2, E3;
  or G1 (T1, A, B, C);
  and G2 (T2, A, B, C);
  and G3 (E1, A, B);
  and G4 (E2, A, C);
  and G5 (E3, B, C);
  or G6 (F2, E1, E2, E3);
  not G7 (F2_not, F2);
  and G8 (T3, T1, F2_not);
  or G9 (F1, T2, T3);
endmodule
```

```
wire F1, F2;
                           ABC = 110 F1 = 0 F2 = 1
parameter stop_time = 100; ABC = 111 F1 = 1 F2 = 1
Circuit_of_Fig_4_2 M1 (F1, F2, D[2], D[1], D[0]);
initial # stop time $finish;
initial begin // Stimulus generator
  D = 3'b000;
  repeat (7) #10 D = D + 1'b1;
end
initial begin //Response monitor
  $display ("A B C F1 F2");
  $monitor ("%b %b %b %b", D[2],
```

Simulation log:

ABC = 000 F1 = 0 F2 = 0ABC = 001 F1 = 1 F2 = 0

ABC = 010 F1 = 1 F2 = 0ABC = 011 F1 = 0 F2 = 1

ABC = 100 F1 = 1 F2 = 0

ABC = 101 F1 = 0 F2 = 1